

Converting a Resistive Input to an Analog Voltage or Current Output

We get many requests for a device to convert a resistance to voltage or current. This can be done very simply using our ARM with voltage divider on the input. We can convert almost any resistive range to a 0-5 VDC signal which can be re-scaled by the ARM to any standard output. The ARM is also capable of re-scaling to most uncommon ranges also (reverse or direct acting).

Standard Outputs

1-5 VDC, 0-10 VDC, 2-10 VDC, 0-15 VDC, 3-15 VDC, 0-20 mA, 4-20 mA.

Uncommon Outputs

0-1 VDC, 4-7 VDC, 0-13 VDC, 2.406-3.868 VDC, 2.635-3.209 VDC, 0-5 mA, 0-10 mA, and many others possible.

Example 1

$P = 20 \text{ VDC}$

$V_{in} = 0-5 \text{ VDC}$

$R_2 = 1000 \text{ ohms (0-1000 ohms)}$

$R_1 = R_2 [(P/V_{in})-1]$

$R_1 = 3000 \text{ ohms}$

$I = E/R = P/(R_1+R_2) = 20/4000 = .005 \text{ amp}$

$\text{Power} = IE = (.005)(20) = .1 \text{ watt}$

$R_1 \text{ wattage needed, } .25 \text{ watt or greater}$

Example 2

$P = 20 \text{ VDC}$

$V_{in} = 0-3.88 \text{ VDC}$

$R_2 = 135 \text{ ohms (0-135 ohms)}$


$R_1 = R_2 [(P/V_{in})-1]$

$R_1 = 560 \text{ ohms}$

$I = E/R = P/(R_1+R_2) = 20/560 = .028 \text{ amp}$

$\text{Power} = IE = (.028)(20) = .56 \text{ watt}$

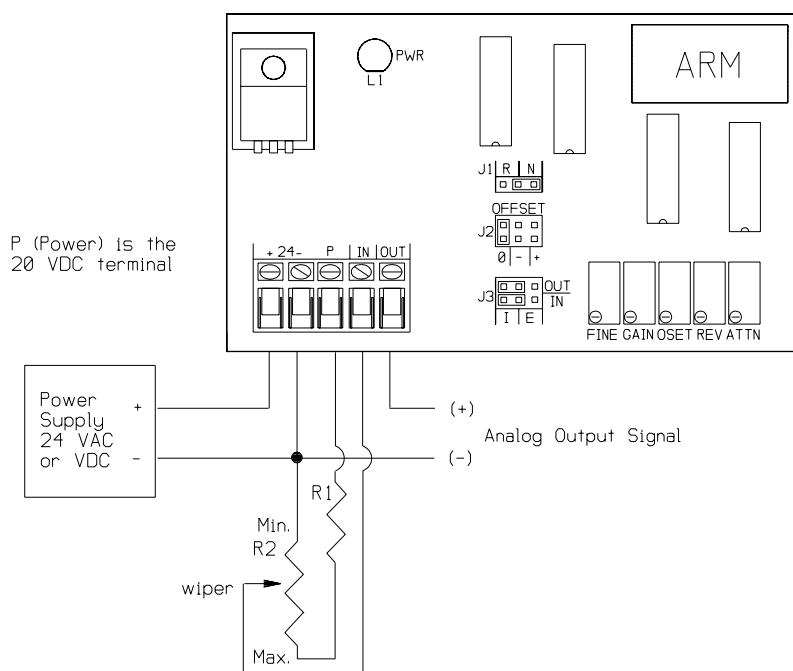$R_1 \text{ wattage needed, } 1/2 \text{ watt or greater}$



The ARM provides a 20 VDC accessory supply voltage that is applied through the series (R1) resistor into the variable resistance output of a controller (R2). This is a voltage divider configuration that will apply a variable analog input into the ARM. It is important to use (R1) for heat dissipation and limiting current.